

Sr. No.	Name	Roll NO	GR. NO
1.	Rachana Patthankar	313035	21910731
2.	Pranali Sapte	313046	21910336
3.	Srushti pokale	313039	21910696
4.	Mahima Mathur	313030	21910745

Q) Design Buck (using LM3524)


$V_{in} = 13.5 - 16.5V$ ,  $V_o = 5V$ ,  $I_o \text{ min} = 0.1A$ ,  $I_o \text{ max} = 1A$ ,  $f_s = 40kHz$ , ( $\Delta I_L = 2 \times I_{o \text{ min}} = 200mA$ )

Ripple = 100 mV p-p,  $I_L \text{ max} = 1.3A$

Efficiency = 80%, Temperature = 0 to 80°C

Step 1: Selection of topology:

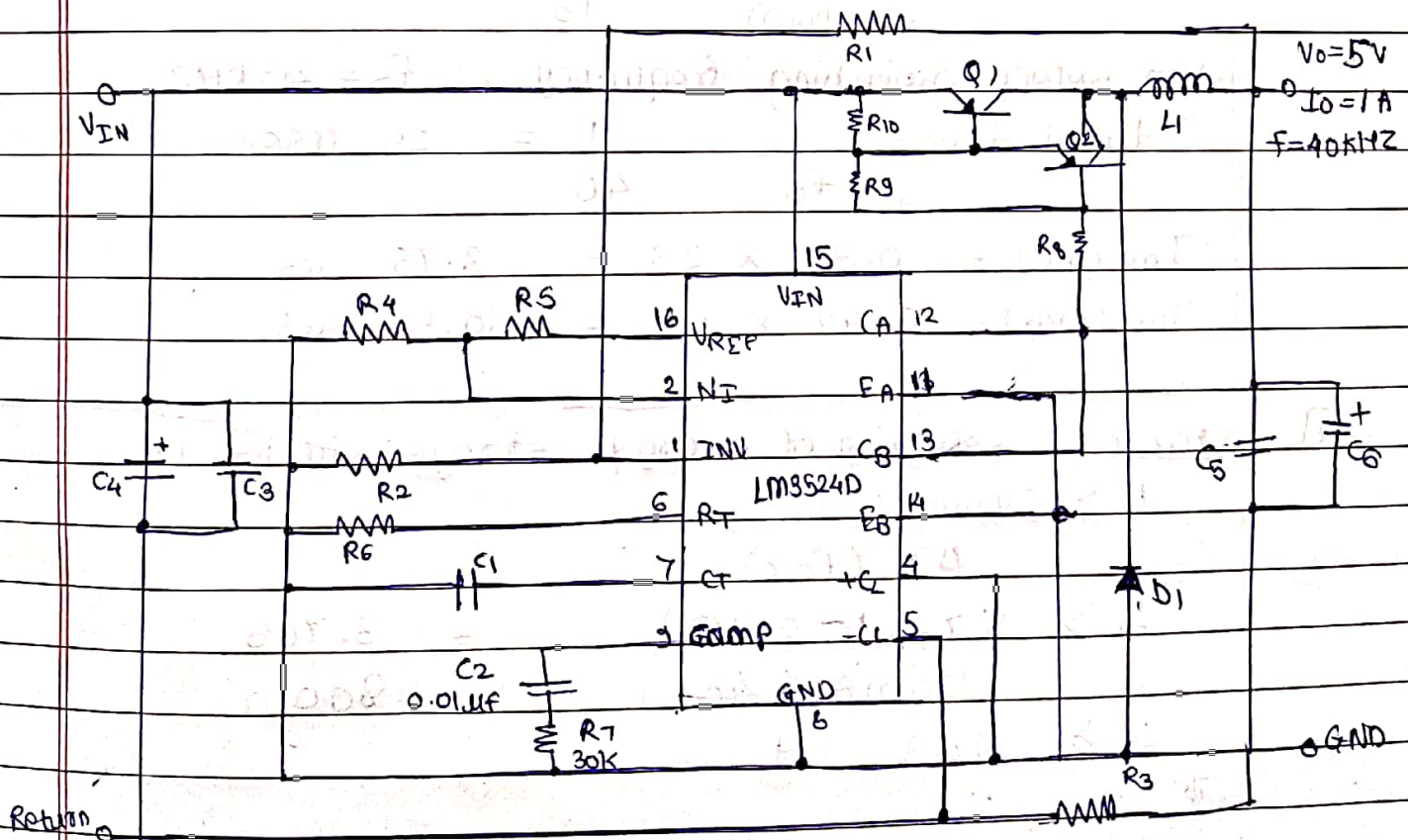consider, Nominal Input Voltage ( $V_{in \text{ nom}}$ ) = 15V



2] Step 2: Calculation of net actual output considering drop across diode & inductor.

Assume voltage drop across diode  $V_d = 0.3$  to  $0.5$  V  
 & Voltage drop across inductor  $V_L = 0.1$  to  $0.2$  V  
 Net o/p voltage ( $V_{net}$ ) =  $V_o + V_{diode} + V_{inductor}$   

$$= 5 + 0.5 + 0.2$$
  

$$= 5.7 \text{ V}$$

3] Step 3: Calculate the required Duty cycle:

①  $D_{(max)} = \frac{V_o}{V_{in(min)}} = \frac{5.7}{13.5} = 0.42$   
 ②  $D_{(min)} = \frac{V_o}{V_{in(max)}} = \frac{5.7}{16.5} = 0.35$   
 ③  $D_{(nom)} = \frac{V_o}{V_{in(nom)}} = \frac{5.7}{15} = 0.38$

We select switching frequency,  $f_s = 40 \text{ kHz}$

$\therefore \text{total time} = \frac{1}{f_s} = \frac{1}{40} = 25 \mu\text{sec}$

$\therefore T_{on(min)} = 0.35 \times 25 = 8.75 \mu\text{s}$

$\therefore T_{on(max)} = 0.42 \times 25 = 10.5 \mu\text{s}$

4] Step 4: selection of energy storage inductor  $L_i$

$$L_i \geq \frac{(V_{net})(1 - D_{min})}{\Delta I_L (f_{osc})}$$

$$L_i \geq \frac{5.7 (1 - 0.35)}{200 \text{ mA} (40 \text{ k})} = \frac{3.705}{8000}$$

$$L_i \geq 463 \mu\text{H}$$

•

$$I_{omax} = (\Delta I_L / 2) + I_o = 1.1 \text{ A}$$

$$L_i \leq \frac{(V_{net})(t_{tr})}{I_{omax}} \times ((D_{max} / D_{Ti}) - 1)$$

( $t_{tr}$  = transient recovery time)



$$D_{\text{max}} > D_T > D_{\text{min}}$$

$$\text{Select } D_T = 0.37$$

$$L \leq \frac{5.7 \times 500 \mu\text{s}}{1} \times \left[ \frac{0.42}{0.37} \right] - 1$$

$$L \leq \frac{560 \mu\text{H}}{350 \mu\text{H}}$$

inductor value  $350 \mu\text{H}$  assuming  $f_{\text{tr}} = 500 \mu\text{s}$

Instead of  $500 \mu\text{s}$ , we select  $1000 \mu\text{s} = 700 \mu\text{H}$

Select inductor value between minimum and maximum value.

$$\text{Let } L = 600 \mu\text{H}$$

Step 4: Calculation of no. of turns of inductor:

$$N = \sqrt{\frac{L}{A_L}} = 22$$

$$A_L = 2750 \text{ nH}$$

$$\therefore N = 22$$

5] Step 5: Selection of filter capacitor.

$$C_0 > \frac{\Delta I_L}{8 \times \Delta V_o \times f_{\text{osc}}} \geq \frac{200 \text{ mA}}{8 \times 0.05 \times 40 \text{ K}} = \frac{200 \text{ mA}}{16 \text{ K}}$$

$$= 12.5 \mu\text{F} \cong 13 \mu\text{F}$$

$$WV_{dc} = 2 \times V_{in \text{ max}}$$

$$\text{calculate ESR of capacitor } \leq \frac{\Delta V_o}{2 \times \Delta I_L} \leq \frac{0.01 \times 5}{2 \times 200 \text{ mA}} \leq 0.125$$

6] Step 6: (Calculations for Pwm Ic LM 3524)

Feedback resistance  $R_1(R_F)$

Assumption, value of  $R_G$  is  $5 \text{ K}$

$$R_F = 5 \text{ K} \cdot 2 \left( \frac{V_o}{2.5} - 1 \right) = 5 \text{ K} \left( \frac{5}{2.5} - 1 \right)$$

$$R_F = 5 \text{ K} \cdot 2$$

Internal voltage available is of 5V.

select values of  $R_4$  &  $R_5 = 5k$ , reference voltage at non inverting terminal of error amplifier is 2.5 Volts

7] Step 7 : current Limiting Resistance  $R_{CL}$  /  $R_3$

current limit Sense Volt

$$R_{CL} = \frac{V_{CL}}{I_{O(max)}}$$

consider, current limit  $V_{CL} = 0.6V$

$$R_{CL} = 0.461 \Omega$$

- Calculate wattages across the  $R_{CL}$

$$P_{R_{CL}} = I_{peak}^2 \times R_{CL}$$

$$= (1.3)^2 \times 0.461 = 0.78 \text{ watt}$$

Select the power watt of resistance  $\geq 2$  Watt

8) Step 8 - Calculations for  $R_T$  ( $R_6$ ) &  $C_T$  ( $C_1$ )

$$f_{osc} \approx \frac{1}{R_T C_T}$$

$$R_T C_T$$

$f_{osc}$  is 40 KHz

Refer  $R_T C_T$  graph from datasheet

$$\text{lets } C_T = 0.01 \mu F$$

$$\text{From datasheet, } R_T = 5k \Omega$$

9] Step 9 :

We can select,

$$R_2 = 5k \Omega, R_4 = 5k \Omega, R_5 = 5k \Omega$$

10] Step 10 : calculation of  $R_8$ ,  $R_9$ ,  $R_{10}$  :

$$I_O = I_{C1} + I_{C2}$$

Initially assume that  $I_{C1} = I_O$

$$\text{So } I_{B1} \approx \frac{I_{C1}}{h_{FE1}}$$



$$I_{E1} = I_{B1} + I_{C1}$$

Assume,  $I_{E2} = I_{B1}$  (i.e. no current is taken from  $R_{10}$  &  $R_9$  branch)

$$\text{So, } I_{B2} \approx \frac{I_{E2}}{h_{FE2}}$$

To calculate  $R_8$ ,

Lets see the branch containing resistance  $R_2$ ,  $R_3$ ,  $R_{10}$

In order to turn on  $Q_1$ , we need the voltage

$V_{BE} > V_{th}$  i.e.  $0.7V$  & current should be greater than base current  $I_B$

Hence,

$$I_{B1} = \frac{I_{C1}}{h_{FE}} = \frac{1A}{20} \quad \therefore \text{consider } h_{FE} = 20$$

condition driving a BJT in saturation  $I_B > I_C / h_{FE}$

$$I_{B1} = 55 \text{ mA}$$

$$I_{B2} \approx \frac{I_{B1}}{h_{FE}} = \left( \frac{55 \text{ m}}{50} \right) \quad \text{consider } h_{FE} = 50$$

$$I_{B2} \approx 1.1 \text{ mA}$$

Let driving current should be  $> 10 \times I$  i.e.  $11 \text{ mA}$

current through  $R_2$  is  $11 \text{ mA}$ . Apply KVL from input,

Voltage across  $R_{10}$ ,  $R_9$ ,  $R_8$  and  $V_{CEsat}$  of internal transistor.

Applying KVL across the  $R_8$ ,  $R_9$ ,  $R_{10}$ ,  $V_{CEsat}$  of internal transistor.

$$\text{Min input voltage} = V_{R_{10}} + V_{R_9} + V_{R_8} + V_{CEsat}$$

$$13.5 = 0.7 + 0.7 + V_{R_8} + 0.2$$

$$V_{R_8} = 11.9 \text{ V}$$

$$R_8 = \frac{V_{R_8}}{I_{R_8}} = \frac{11.9}{11 \text{ mA}}$$

$$R_8 = 1 \text{ k}\Omega$$

$R_9$  &  $R_{10}$  can be found by just voltage divider circuit

$$\therefore \text{Hence } R_9 = R_{10} = 100 \Omega$$

Verification :

- current in  $R_9$  &  $R_{10}$  branch is  $0.7/100 \Omega = 7 \text{ mA}$
- current assumed through  $R_8$  is  $11 \text{ mA}$ .
- $I_{B2} = 11 - 7 = 4 \text{ mA}$ , still  $I_{B2}$  is  $(1/0.1) = 3.63$  times  $I_{B1}$ .  $h_{fe2}$  &  $q_2$  will be well driven into saturation.